

Total number of printed pages-02

2(Sem-8/FYUGP)BNC(A)/DSCI

2025

Computer Science

(Discipline Specific Core)

Paper Name: Digital Logic Fundamentals

Paper Code: BCA-DSC-145

Full Marks: 60

Time: Two and Half Hours

(The figures in the margin indicate full marks for the questions)

Answer in English

- 1. Answer the following questions as directed: 1x7=7**
 - a) Write the full form of ASCII.
 - b) What is a Flip Flop?
 - c) What is an inverter?
 - d) Which logic gate is known as Universal Gate and why?
 - e) Write the De-Morgan theorem.
 - f) What is combinational circuit
 - g) What do you mean by binary numbers.

- 2. Answer any four of the following questions: 2x4=8**
 - a) What is ROM?
 - b) What do you mean by minterm and maxterm?
 - c) Convert $(100101)_2$ to decimal number.
 - d) What is shift register?
 - e) What is binary number system?

3. Answer the following questions (any three): **5x3=15**

- a) Explain multiplexer with logic diagram.
- b) Explain Full Adder with truth table and circuit diagram.
- c) Briefly explain the J-K flip-flop with circuit diagram.
- d) Simplify the Boolean function using K-Map,
 $F(W,X,Y,Z) = \sum(1,3,7,11,15)$ with Don't care
 $d(w,x,y,z) = \sum(0,2,5)$
- e) Find the complement of Boolean functions.
(i) $F1 = x' yz' + x' y'z$ (ii) $F2 = x(y'z' + yz)$

4. Answer any three of the following questions: **10x3=30**

- a) What is counter? Design a 3-bit binary counter and give logic diagram.
- b) What is digital system? Write characteristics of digital system.
- c) What is an Encoder? Explain Octal to Binary Encoder with proper diagram and function table.
- d) Explain different postulates and basic theorems of Boolean algebra with example.
- e) For a 3-bit shift register explain the operation for serial in serial out shift.
