

Total number of printed pages-7

1 (Sem-4) PHY 3

2025

PHYSICS

Paper : PHY0400304

(Analog Electronics)

Full Marks : 45

Time : 2 hours

The figures in the margin indicate full marks for the questions.

1. Answer the following questions : $1 \times 5 = 5$
- (a) What is the output frequency of a full wave rectifier where input frequency is 100Hz?
 - (b) In _____ amplifier, the collector current flows for less than half cycle of the input signal.
 - (c) What type of amplifier is used to reject hum and static voltage induced into its input leads?

- (d) The change in the output wave shape from input wave shape in an amplifier is called _____.
- (e) State the biasing method of a photodiode.

2. Answer the following questions : **(any five)**
 $2 \times 5 = 10$

- (a) Why does the frequency response of a RC coupled amplifier decrease with increasing frequency after cutoff?
- (b) How is electrostatic deflection caused in a CRO?
- (c) What happens when the feedback resistance of an operational amplifier is replaced by a (i) capacitor (ii) diode? Write an expression for the output voltage in each case.
- (d) Why is a diode called a non-linear device?
- (e) Define CMRR. What is the significance?
- (f) Explain Q point of a transistor.
- (g) What is static and dynamic resistance of a diode?

- (h) State the principle behind light emitting diodes..
- (i) State the role of coupling capacitors and bypass capacitor in a two state stage RC coupled amplifiers.
- (j) State the characteristics of an ideal Op-Amp.

3. Answer the following questions : **(any four)**
 $5 \times 4 = 20$

- (a) $1 + 2 + 2 = 5$
- (i) Draw the circuit diagram of a full wave rectifier circuit with a filter.
- (ii) Draw and explain the nature of signal at various stages.
- (iii) A power supply A delivers 15V DC with a ripple of $0.6 V_{rms}$ while another power supply B delivers 20V DC with a ripple of $2m V_{rms}$. Which power supply is better and why?
- (b) $1 + 1 + 3 = 5$
- (i) Define faithful amplification of a transistor amplifier.
- (ii) How is faithful amplification obtained in CE configuration?

- (iii) Draw the characteristics of a transistor amplifier and show the active, cutoff and saturation region. Why does these region's occur?
- (c) How does negative feedback effect the input and output impedance of an amplifier? How is the change profitable in practice? $2+3=5$
- (d) $2+2+1=5$
- (i) What is Barkhausen Criteria for continuous undamped oscillations?
- (ii) How is this criteria met in RC phase-shift oscillator?
- (iii) A phase-shift oscillator uses $10pF$ capacitor. Find the value of R to produce a frequency of $1000kHz$.
- (e) $2+2+1=5$
- (i) Draw the characteristic of Zener diode. How does this differ from a normal diode?
- (ii) On what does the breakdown voltage depend on and how can this voltage be changed?
- (iii) How is a Zener diode biased and why?

(f) Why is CE configuration used in 90-95% of all the transistor applications?

(g) A sinusoidal signal whose amplitude is $1V$ is applied at the input terminals of

(i) An inverting amplifier of $R_I = 1k\Omega$, $R_F = 2k\Omega$.

(ii) A non-inverting amplifier with $R_I = 1k\Omega$, $R_F = 2k\Omega$.

(iii) A comparator circuit.

Draw the output in each case if R_F is the feedback resistance and the power supply is $V_{CC} = \pm 10V$. What is the function of negative feedback from the analysis? $3+2=5$

(h) $1+1+3=5$

(i) What is $3dB$ frequency or half power frequency?

(ii) What does half power frequency denote?

(iii) Explain the condition of distortionless amplification based on frequency response.

4. Answer the following questions : **(any one)**
10

- (a) 2+3+5=10
- (i) What is stabilization in amplifiers?
 - (ii) Why is stabilization required? Explain.
 - (iii) Compare stability of Fixed Bias and Voltage Divider bias explaining the reason behind this.

- (b) 5+5=10
- (i) How does the energy band diagram of a $P-N$ junction change in forward bias and reverse biased condition?
 - (ii) How is the current across the junction caused for the two conditions? Explain with required diagrams.

- (c) 2+3+5=10
- (i) What are h parameters?
 - (ii) Draw the h parameter equivalent circuit for a CE configuration.
 - (iii) Find expressions for input and output impedance of an amplifier as a function of the h parameter.

(d) 2+2+6=10

- (i) Define Slew Rate of an OP-AMP.
- (ii) What is the use of slew rate in applications of OP-AMPs?
- (iii) It is required to design a circuit using OP-AMP to obtain the output

$$V_{out} = (2V_1 + 3V_2 - 4V_3)$$

draw a circuit to obtain the output if V_1 , V_2 and V_3 are the inputs.